

PHYSICS

Class - XII

CURRENT ELECTRICITY
- II



पुर्णमा International School

Shree Swaminarayan Gurukul, Zundal


CURRENT ELECTRICITY - II

1. Kirchhoff's Laws of electricity
2. Wheatstone Bridge
3. Metre Bridge
4. Potentiometer
 - i) Principle
 - ii) Comparison of emf of primary cells

KIRCHHOFF'S LAWS:

I Law or Current Law or Junction Rule:

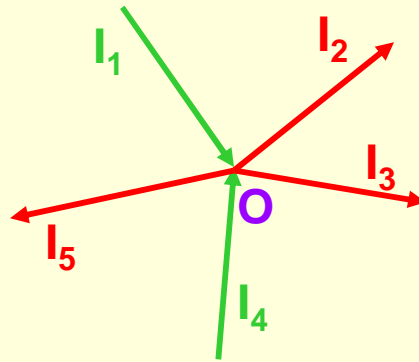The algebraic sum of electric currents at a junction in any electrical network is always zero.



$$I_1 - I_2 - I_3 + I_4 - I_5 = 0$$


Sign Conventions:

1. The **incoming currents** towards the junction are taken **positive**.
2. The **outgoing currents** away from the junction are taken **negative**.

Note: The charges cannot accumulate at a junction. The number of charges that arrive at a junction in a given time must leave in the same time in accordance with conservation of charges.

II Law or Voltage Law or Loop Rule:

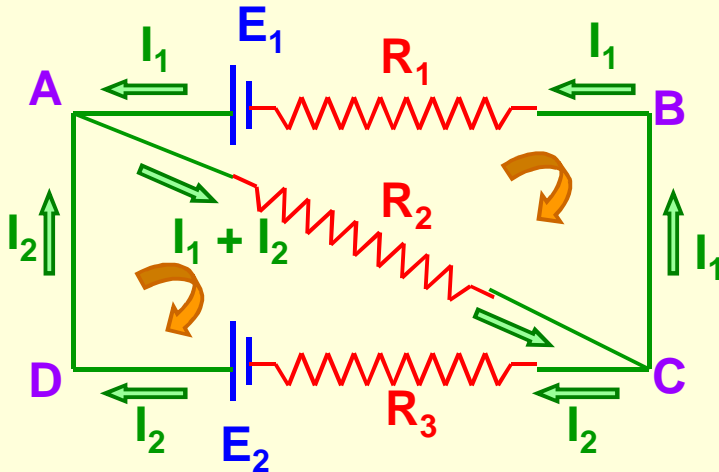The algebraic sum of all the potential drops and emf's along any closed path in an electrical network is always zero.



Loop ABCA:

$$- E_1 + I_1 \cdot R_1 + (I_1 + I_2) \cdot R_2 = 0$$

Loop ACDA:

$$- (I_1 + I_2) \cdot R_2 - I_2 \cdot R_3 + E_2 = 0$$

Sign Conventions:

1. The emf is taken **negative** when we traverse from **positive to negative** terminal of the cell through the electrolyte.
2. The emf is taken **positive** when we traverse from **negative to positive** terminal of the cell through the electrolyte.

The potential **falls** along the direction of current in a current path and it **rises** along the direction opposite to the current path.

3. The potential **fall** is taken **negative**.
4. The potential **rise** is taken **positive**.

Note: The path can be traversed in clockwise or anticlockwise direction of the loop.

Wheatstone Bridge:

Currents through the arms are assumed by applying Kirchhoff's Junction Rule.

Applying Kirchhoff's Loop Rule for:


Loop ABDA:

$$-I_1 \cdot P - I_g \cdot G + (I - I_1) \cdot R = 0$$

Loop BCDB:

$$-(I_1 - I_g) \cdot Q + (I - I_1 + I_g) \cdot S + I_g \cdot G = 0$$

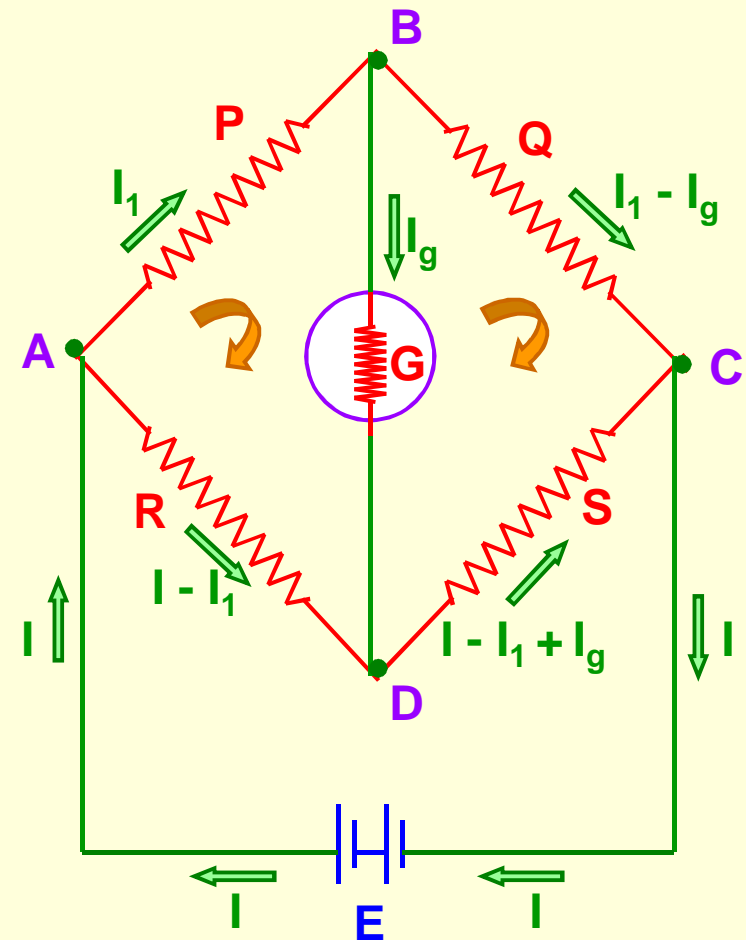When $I_g = 0$, the bridge is said to be balanced.




By manipulating the above equations, we get

$$\frac{P}{Q} = \frac{R}{S}$$

Metre Bridge:

Metre Bridge is based on the principle of Wheatstone Bridge.

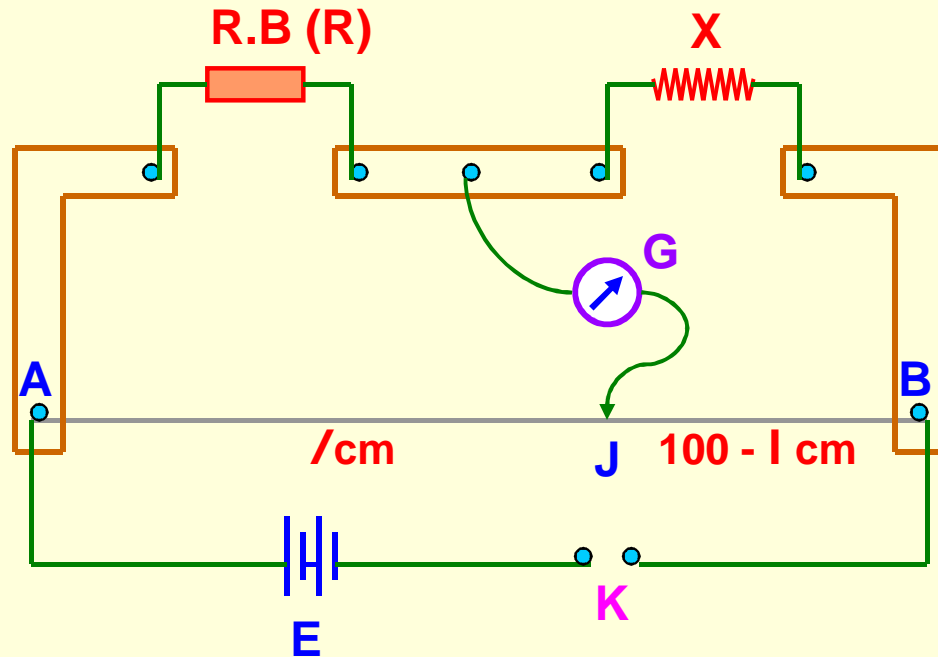When the galvanometer current is made zero by adjusting the jockey position on the metre-bridge wire for the given values of known and unknown resistances,



$$\frac{R}{X} = \frac{R_{AJ}}{R_{JB}} \quad \longrightarrow \quad \frac{R}{X} = \frac{AJ}{JB} \quad \longrightarrow \quad \frac{R}{X} = \frac{l}{100 - l}$$

(Since, Resistance \propto length)

Therefore, $X = R (100 - l) / l$

Potentiometer:

Principle:



$$V = I R$$
$$= I \rho l / A$$

If the constant current flows through the potentiometer wire of uniform cross sectional area (A) and uniform composition of material (ρ), then

$$V = KI \quad \text{or} \quad V \propto I$$

V / I is a constant.

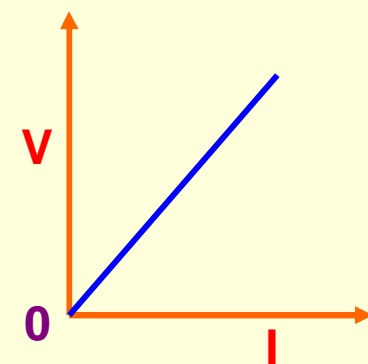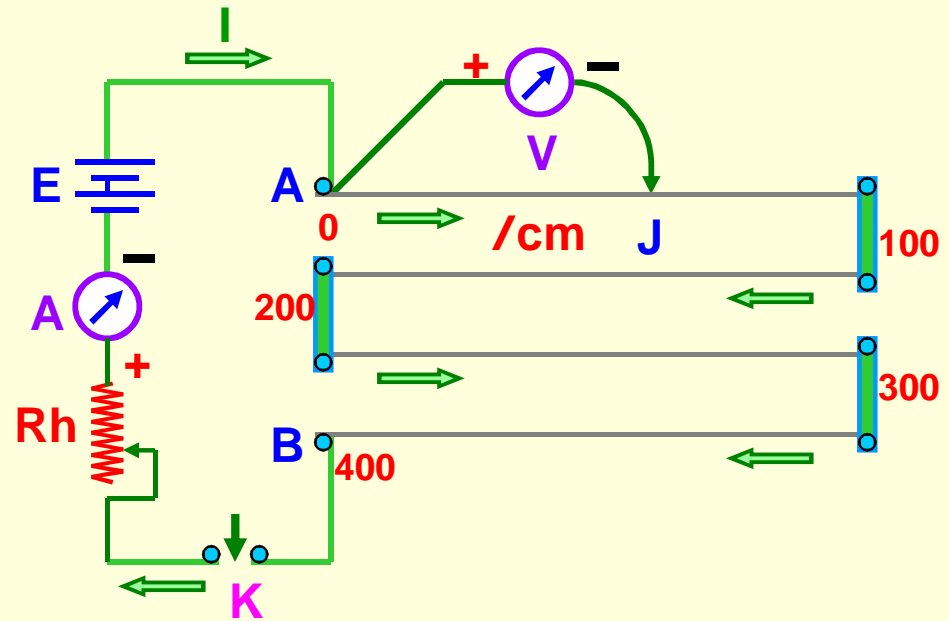The potential difference across any length of a wire of uniform cross-section and uniform composition is proportional to its length when a constant current flows through it.



Comparison of emf's using Potentiometer:

The balance point is obtained for the cell when the potential at a point on the potentiometer wire is equal and opposite to the emf of the cell.

$$E_1 = V_{AJ_1} = I \rho l_1 / A$$

$$E_2 = V_{AJ_2} = I \rho l_2 / A$$

$$E_1 / E_2 = l_1 / l_2$$

Note:

The balance point will not be obtained on the potentiometer wire if the fall of potential along the potentiometer wire is less than the emf of the cell to be measured.

The working of the potentiometer is based on null deflection method. So the resistance of the wire becomes infinite. Thus potentiometer can be regarded as an ideal voltmeter.

